
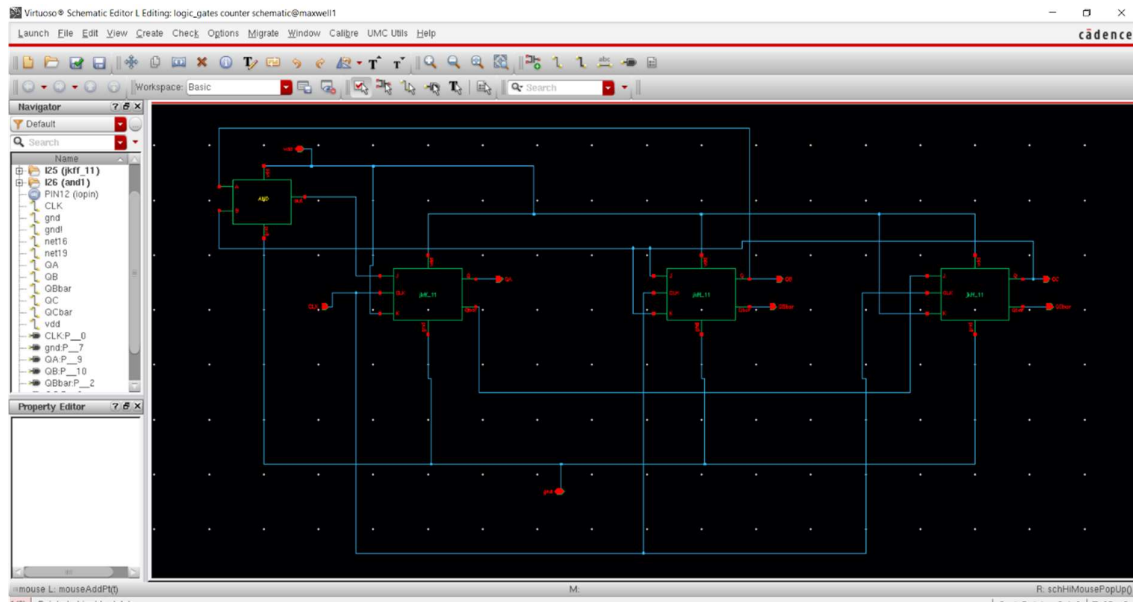


## MOD-5 COUNTER USING JK FLIP FLOP

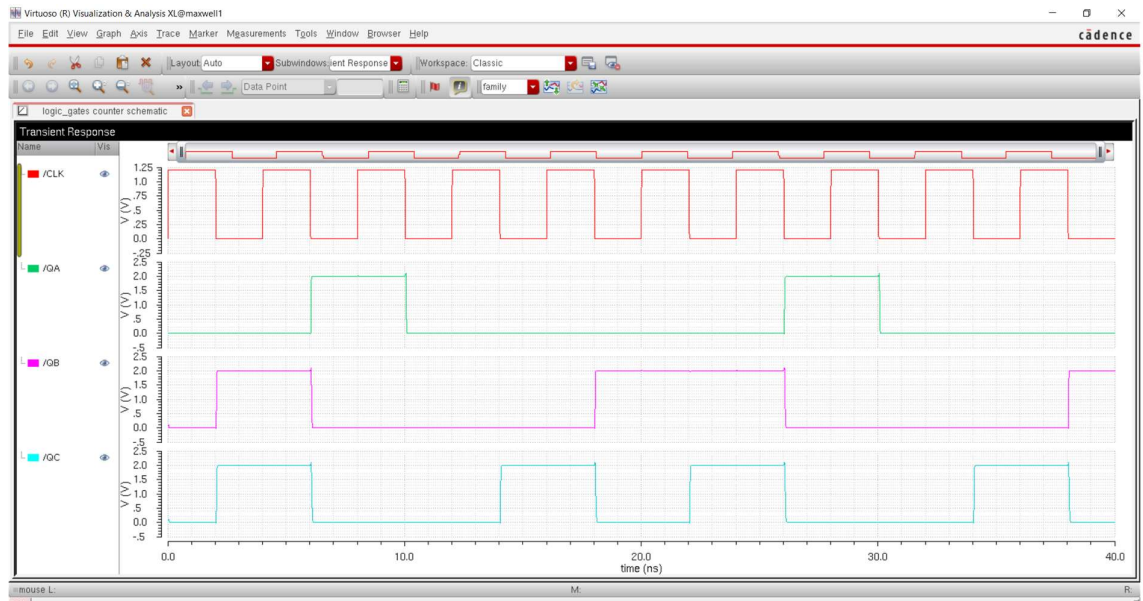


Output at different frequencies:

(i) 250MHz




Calculation of fall time:

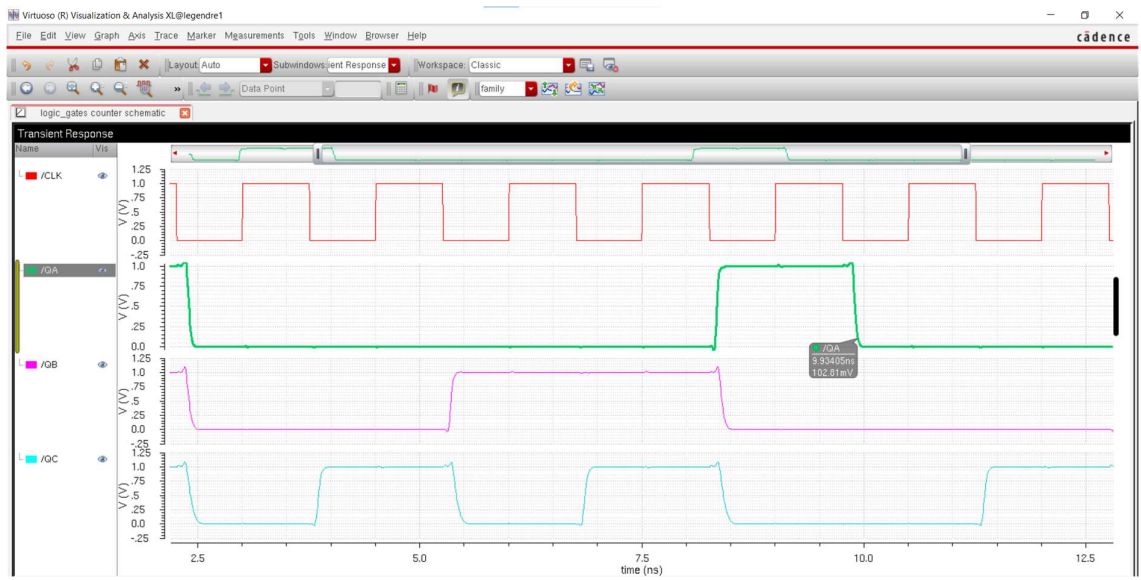

Fall time= 9.93405ns - 9.88052ns = 0.05353ns

## Calculation of Rise time:

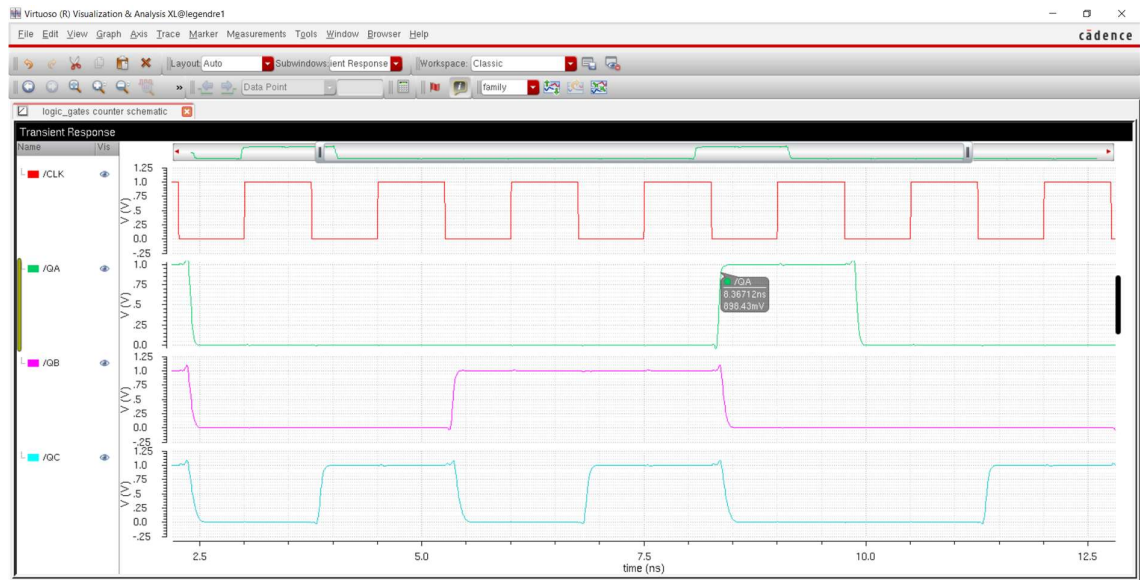

$$\text{Rise Time} = 8.36712\text{ns} - 8.32916\text{ns} = 0.03796\text{ns}$$

(ii)333MHz

